

**Higher Secondary (Vocational)**

**CLASS XI**

**Semester - 1**

**Basic Electrical Theory**

**Time Allowed: 45 Mins**

**Full Marks: 20**

A. Choose the correct alternative from the following

1. Kilo watt hour is the unit of i) energy; ii) power; iii) electric charge; iv) electric current.
2. A semi- conductor is formed by i) covalent bond; ii) electrovalent bond; iii) coordinate; iv) none of these.
3. Addition of trivalent impurity to a pure semi-conductor material creates many \_\_\_\_  
i) valance electron; ii) free electron; iii) holes; iv) bound electron.
4. Two lamps, 100 W, 250 V and 200 W, 250 V are connected in parallel across a 500 V line. Then i) 100 W lamp will fuse; ii) 200 W lamp will fuse; iii) both the bulbs will fuse; iv) nolamp will be fuse.
5. Two electric lamps of 40 W are connected in parallel. The power consumed by the combination is i) 20W; ii) 40 W; iii) 80W; iv) 100 W.
6. In which of the following substances the resistance decreases with increase in temperature? I) carbon; ii) constantan; iii) copper; iv) silver.
7. A passive circuit element in a circuit is one which \_\_. I) supplies energy; ii) receives energy; iii) both supplies and receives energy; iv) none of these.
8. Energy stored in a 2 H inductor when carrying a current of 4 A is i) 16 W; ii) 8 W; iii) 10 W; iv) 32 W.
9. Two numbers of 2 micro farad capacitors are connected in series , the equivalent capacitance will be i) 2 micro farad; ii) 4 micro farad; iii) 1 micro farad; iv) 3 micro farad.
10. A sinusoidal voltage  $v = 10 \sin 314 t$ , the time period of the voltage i) 0.02 sec; 0.2 sec; iii) 0.01 sec; iv) 50 sec.
11. For a sinusoidal current having maximum value of 10 A, the corresponding rms value will be i) 7.07A; ii) 5.77 A; 10 A; iv) 9.09A.
12. The form factor of a sinusoidal quantity is given by i) RMS value/ Average value; ii) Average value/ RMS value; iii) Maximum value/ RMS value; iv) RMS value/ Maximum value.
13. The peak factor of an sinusoidal quantity is given by i) Maximum value/ RMS value; ii)RMS value/ Maximum value; iii) Average value / maximum value; iv) maximum value / Average value;
14. A 10 V d.c source is connected in series with two resistances of 4  $\Omega$  and 6  $\Omega$ . The current through the circuit will be i) 1 A; ii) 2.5 A; iii) 1.67 A; iv) 4.2A.

15. An inductor  $L$  is connected in series with an ac supply having frequency of  $f$  Hz. The inductive reactance of the circuit is given by i)  $2\pi fL$ ; ii)  $\frac{1}{2\pi fL}$  iii)  $\pi fL$ ; iv) none of these.
16. In a circuit, at a node three branches meet. The node has an incoming current of 5 A and outgoing current of 6 A from two of these branches. The third branch will have an: i) incoming current of 5 A; ii) outgoing current of 5 A; iii) incoming current of - 1 A; iv) outgoing current of -1 A.
17. Kirchoff's law is applicable for i) passive network; ii) A.C. Network; iii) d.c. network; iv) Both A.C. and D.C network.
18. In an electrical network, for any closed loop, the algebraic summation of voltages is i) zero; ii) always one; iii) one or more than one; iv) one or less than one.
19. A junction or a point where two (or more) network elements intersect is called as i) Node; ii) Branch; iii) Loop; iv) Mesh.
20. What number of equations will be needed to solve the network in nodal analysis if there are a total of 'N' nodes in the circuit? i)  $N-1$ ; ii)  $N+1$ ; iii)  $N$ ; iv)  $N-2$

**ANSWER KEY**

<b>1</b>	i	<b>2</b>	ii	<b>3</b>	iii	<b>4</b>	iii	<b>5</b>	iii
<b>6</b>	i	<b>7</b>	ii	<b>8</b>	i	<b>9</b>	iii	<b>10</b>	i
<b>11</b>	i	<b>12</b>	i	<b>13</b>	i	<b>14</b>	i	<b>15</b>	i
<b>16</b>	iv	<b>17</b>	iv	<b>18</b>	i	<b>19</b>	i	<b>20</b>	i